

Understanding eFuse Input Voltage Transients from Hot Plug Events

How to Determine if an eFuse System Can be Safely Hot-Plugged

AND90059/D

INTRODUCTION

System designers must account for voltage surges that occur when supplies or loads are connected. eFuses are integrated circuits with many features to protect loads from these surges. However, it is important to ensure that the eFuse itself will not receive excessive voltage on its input. This application note uses mathematical calculations, simulations, and actual lab data to illustrate the voltage surge as an eFuse is suddenly connected on the input side. System designers can use this information to make certain that the eFuse will be within its limits.

Basic System Layout

The maximum input voltage of an eFuse is always specified on the datasheet. An eFuse may not be damaged by a voltage above the maximum specified on the datasheet, but it could be dangerous depending on the circumstances. Figure 1 helps visualize the issue. During a hot plug on the input, the voltage may enter either the blue or red zone depending on variables. These variables include:

- DC supply voltage level
- Maximum eFuse input voltage
- Resistance, inductance, and capacitance (RLC) values
- Presence of a protection device like a Zener diode

A diagram of a system where these voltage levels can appear is shown in Figure 2. There is a detachable cable

between the DC voltage supply and the eFuse that allows a user to quickly switch supplies or circuit boards. Any circuitry downstream of the eFuse (i.e. on the output side) will be protected by the eFuse and its protection features during the input hot plug. The system diagram can be broken down into an electrical schematic with R, L, and C components for analysis.

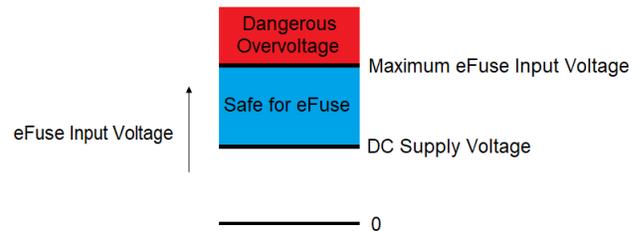


Figure 1. Important Voltage Levels in a System with an eFuse

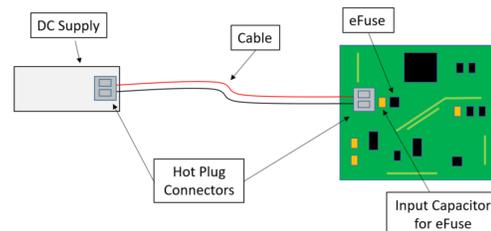


Figure 2. System Diagram

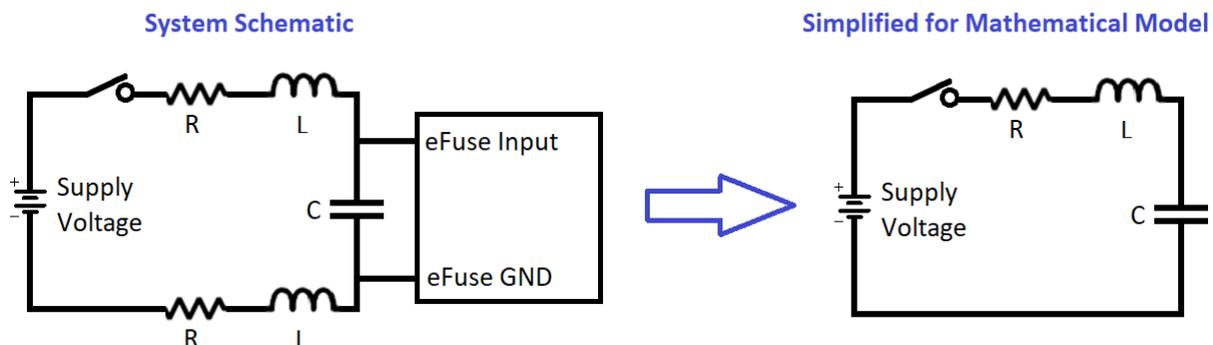


Figure 3. The System Schematic is Converted to a Simplified Series RLC Circuit since the eFuse can be Considered High Impedance. Also since the Positive and GND Return Cables are in Series they can be Lumped Together

Calculations and Spreadsheet Tool

The electrical schematic with R, L, and C components and a DC supply is shown on the left side of Figure 3. The voltage across the capacitor is the voltage that will appear at the input of the eFuse. A simplified model is shown on the right side of Figure 3. To generate the simplified model, the series components are lumped together, the eFuse output voltage is ignored (the eFuse has a delay circuit to keep the output disconnected during the hot plug), and the very small (< 1 mA) eFuse input to GND bias current that powers the eFuse’s controller is ignored.

The equation that describes the voltage across the capacitor in this circuit is:

$$v_c(t) = V_{supply} - (V_{supply}) \left[\exp(\sigma t) \left(\cos(\omega_d t) - \frac{\sigma}{\omega_d} \sin(\omega_d t) \right) \right]$$

$$\sigma = \frac{-R}{2L}, \omega_d = \sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}$$

A mathematical model was created. This can be done with software such as Microsoft Excel or MATLAB. The following case was tested:

DC Supply (V)	R (Ω)	L (H)	C (F)
30	0.1	5E-07	1E-06

Figure 4 shows the capacitor voltage vs. time. Although the DC supply voltage was only 30 V, the peak capacitor voltage was 54 V.

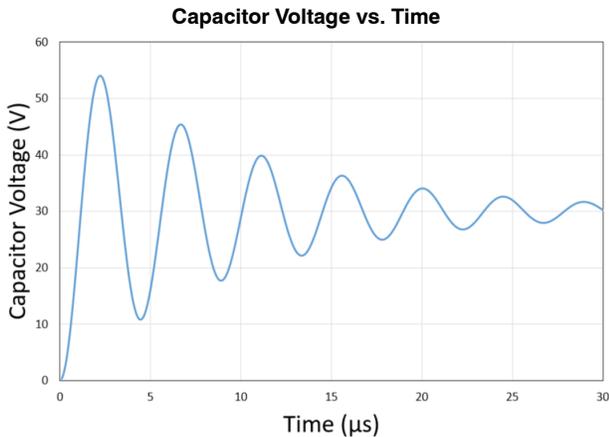


Figure 4. Result from Mathematical Model

Simulations

Simulation software can be used to model the waveform. The schematic is shown below in Figure 5.

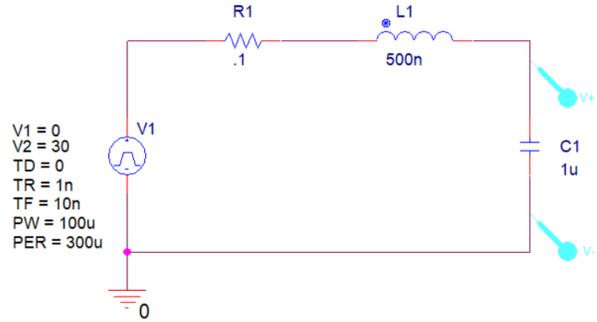


Figure 5. Simulation Schematic

The result in Figure 6 can be compared to that from the mathematical model in Figure 4. Note that the $V_C(t)$ response is almost identical between the mathematical model and the simulation.

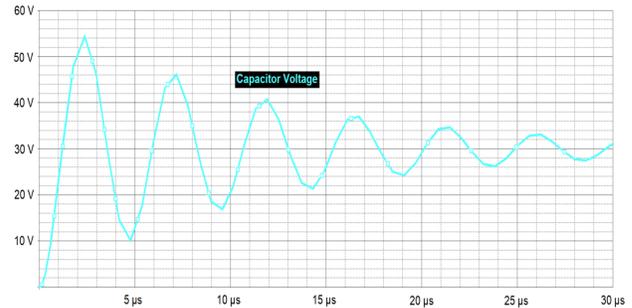


Figure 6. Simulation Result

Lab Measurements

A lab measurement was taken to corroborate the mathematical model and simulation results. A 12”, 18 gauge banana cable was used. The inductance and resistance of the combination of the power supply and cable were 500 nH and 120 mΩ. There were some additional parasitics in the capacitor that were not measured, but the values were considered close enough for corroboration to the results presented from the mathematical model and simulations in Figures 4 and 6. The capacitor was a 1 μF, 50 V ceramic type (part number: FK20X7R1H105K by TDK Corporation). The power supply was an Extech 382275. The power supply’s internal output capacitance near the terminals is very large (more than 800 μF), which is a nearly ideal DC supply.

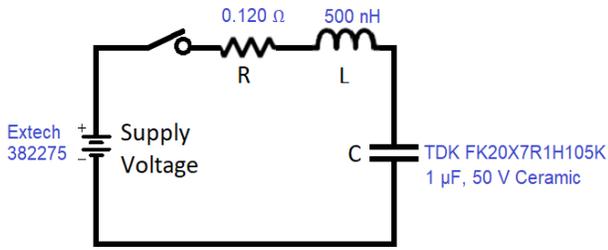


Figure 7. Lab Measurement Circuit

The peak voltage and oscillation frequency showed a close match to the mathematical result in Figure 4 and the simulation result in Figure 6.

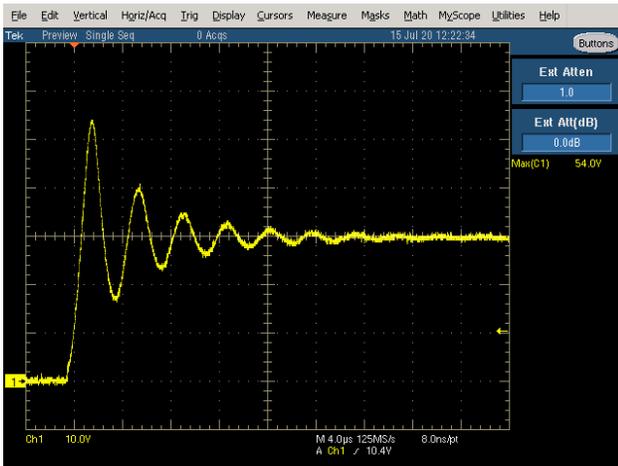


Figure 8. Lab Measurement Hot Plugging into a 1 μF Capacitor Only (no eFuse)

Next, an eFuse was connected to check if the presence of the eFuse would change the $V_C(t)$ waveform. An NIS5420 eFuse was connected in parallel with the capacitor. Comparing Figures 8 and 9, the results are indistinguishable and it is clear that the eFuse does not change the $V_C(t)$ result.

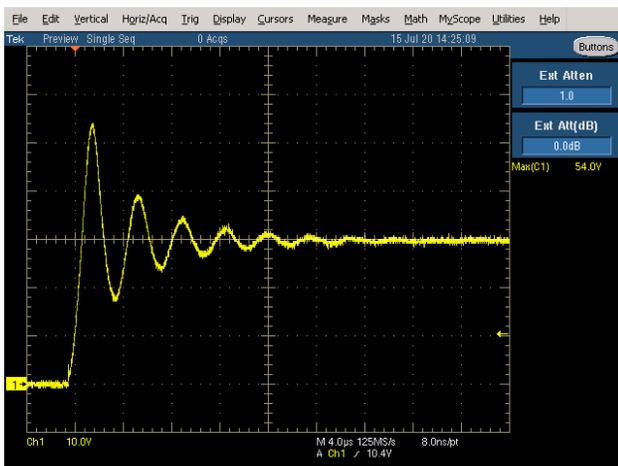


Figure 9. Lab Measurement with 1 μF Capacitor and an NIS5420 eFuse Connected in Parallel

Additional Test Cases

Several other RLC combinations were tested using the mathematical model and simulations and the results are shown in the Table 1 below. % Surge is the additional voltage above the supply voltage that appears across the capacitor. Note that the max capacitor voltage (Max V_C) is never more than twice the supply voltage.

Table 1. ADDITIONAL TEST CASES

Case	DC Voltage (V)	R (Ω)	L (H)	C (F)	Max V_C (V)	% Surge	Peak Current (A)
1	30	0.1	5.00E-07	1.00E-06	54	80	38
2	30	0.1	5.00E-07	1.00E-05	45	50	99
3	30	0.1	5.00E-07	1.00E-04	31	3	193
4	30	0.1	2.00E-06	1.00E-06	57	90	20
5	30	0.1	2.00E-06	1.00E-05	51	70	57
6	30	0.1	2.00E-06	1.00E-04	39	30	134
7	30	0.1	5.00E-06	1.00E-06	58	93	13
8	30	0.1	5.00E-06	1.00E-05	54	80	38
9	30	0.1	5.00E-06	1.00E-04	43	43	98
10	30	0.3	5.00E-07	1.00E-06	45	50	32
11	30	0.3	5.00E-07	1.00E-05	32	7	63
12	30	0.3	5.00E-07	1.00E-04	30	0	88
13	30	0.3	2.00E-06	1.00E-06	51	70	18
14	30	0.3	2.00E-06	1.00E-05	40	33	43
15	30	0.3	2.00E-06	1.00E-04	30	0	75
16	30	0.3	5.00E-06	1.00E-06	54	80	12
17	30	0.3	5.00E-06	1.00E-05	45	50	32
18	30	0.3	5.00E-06	1.00E-04	30	0	63
19	30	0.5	5.00E-07	1.00E-06	39	30	27
20	30	0.5	5.00E-07	1.00E-05	30	0	46
21	30	0.5	5.00E-07	1.00E-04	30	0	56
22	30	0.5	2.00E-06	1.00E-06	47	57	17
23	30	0.5	2.00E-06	1.00E-05	34	13	35
24	30	0.5	2.00E-06	1.00E-04	30	0	52
25	30	0.5	5.00E-06	1.00E-06	51	70	11
26	30	0.5	5.00E-06	1.00E-05	39	30	27
27	30	0.5	5.00E-06	1.00E-04	30	0	46

Max capacitor voltage (V_C) was plotted individually against R, L, and C. Figures 10–12 correspond to parameters of Table 1. These figures show that larger voltage surges correspond to lower resistance, lower capacitance, and higher inductance.

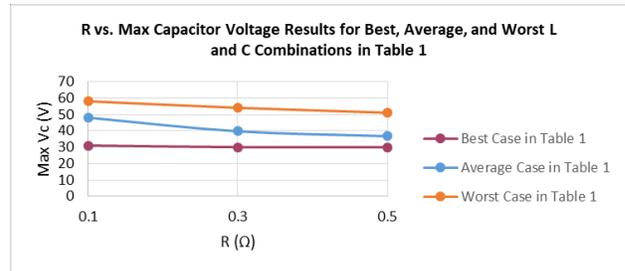


Figure 10. R vs. Average Max Capacitor Voltage

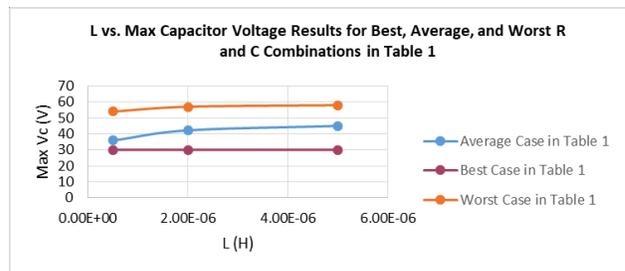


Figure 11. L vs. Average Max Capacitor Voltage

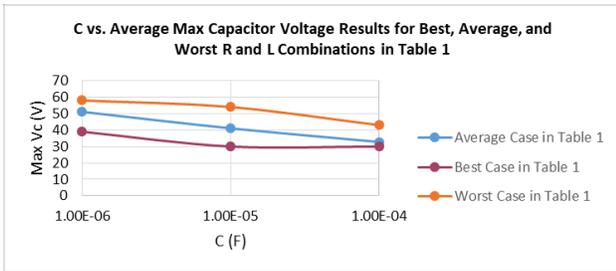


Figure 12. C vs. Average Max Capacitor Voltage

Inrush current can also be a consideration. The peak inrush current can be obtained simply by using the $i = C \cdot dv/dt$ equation. Although higher capacitance helps suppress the voltage, it will draw additional inrush current. For example, in Table 1, with the large 100 μ F capacitor the inrush current ranged from 46 to 193 A depending on the R and L values.

One way to lower the voltage spike without increasing the inrush current is to use an external Zener diode. A test was done with a 33 volt zener (part number: MMBZ5257B by onsemi) using the same bench test setup.

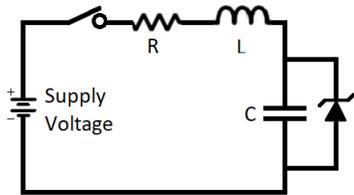


Figure 13. Addition of Zener Diode

Although the nominal value of the Zener was 33 V, the peak voltage reached 48 V because of the resistive nature of the Zener when there is high current.

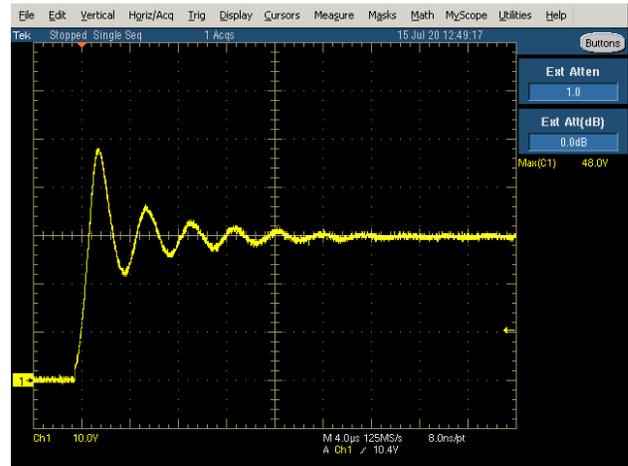


Figure 14. Voltage Spike was Reduced from 54 to 48 V with the Addition of the 33 V Zener Diode

Summary

During a hot plug event on the input, the eFuse input voltage may reach a level that is twice the DC supply voltage. A larger capacitor or Zener diode at the input can help keep the eFuse input voltage at a safe level.

onsemi, Onsemi, and other names, marks, and brands are registered and/or common law trademarks of Semiconductor Components Industries, LLC dba "onsemi" or its affiliates and/or subsidiaries in the United States and/or other countries. onsemi owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of onsemi's product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. onsemi reserves the right to make changes at any time to any products or information herein, without notice. The information herein is provided "as-is" and onsemi makes no warranty, representation or guarantee regarding the accuracy of the information, product features, availability, functionality, or suitability of its products for any particular purpose, nor does onsemi assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using onsemi products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by onsemi. "Typical" parameters which may be provided in onsemi data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. onsemi does not convey any license under any of its intellectual property rights nor the rights of others. onsemi products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use onsemi products for any such unintended or unauthorized application, Buyer shall indemnify and hold onsemi and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that onsemi was negligent regarding the design or manufacture of the part. onsemi is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

PUBLICATION ORDERING INFORMATION

LITERATURE FULFILLMENT:
Email Requests to: orderlit@onsemi.com

TECHNICAL SUPPORT
North American Technical Support:
Voice Mail: 1 800-282-9855 Toll Free USA/Canada
Phone: 011 421 33 790 2910

Europe, Middle East and Africa Technical Support:
Phone: 00421 33 790 2910
For additional information, please contact your local Sales Representative